 


Verilog Language Features

- Explicit Association Example - Full Adder Using Half Adder Module



```
module half_adder (Sum, Carry, A, B);
```

```
module full_adder (Sum, Cout, A, B, Cin);  
    input A, B, Cin;  
    output Cout, Sum;  
    wire w1, w2, w3;  
    half_adder HA1 (.A(A), .B(B), .Sum(w1), .Carry(w2));  
    half_adder HA2 (.Sum(Sum), .Carry(w3), .B(Cin), .A(w1));  
    or (Cout, w2, w3);  
endmodule
```

Ports are explicitly
specified - order is
not important

Less chance for errors


Verilog Language Features

Combinational vs. Sequential Circuits

Combinational: The output only depends on the present input.



 Sequential: The output depends on both the present input and the previous output(s) (the state of the circuit).



Verilog Language Features

Combinational vs. Sequential Circuits

Sequential logic: Blocks that have memory elements: Flip-Flops, Latches, Finite State Machines.

- Triggered by a 'clock' event.
 - Latches are sensitive to level of the signal.
 - Flip-flops are sensitive to the transitioning of clock

Combinational constructs are not sufficient. We need new constructs:

- **always**
- **initial**

```
always @ (sensitivity list)  
    statement;
```

Verilog Language Features

Sequential Circuits

```
always @ (sensitivity list)  
statement;
```

Whenever the event in the sensitivity list occurs, the statement is executed.



Remember our
counter example

```
module simple_counter(clk, rst, count);  
    input clk, rst;  
    output [31:0] count;  
    reg [31:0] count;  
  
    always @(posedge clk)  
    begin  
        if(rst)  
            count = 32'b0;  
        else  
            count = count + 1;  
    end  
endmodule
```

Verilog Language Features

Sequential Circuits

- Sequential statements are within an **'always'** block,
- The sequential block is triggered with a change in the sensitivity list,
- Signals assigned within an **always** block must be declared as **reg**,
 - The values are preserved (memorized) when no change in the sensitivity list.
- We do not use **'assign'** within the **always** block.

■ Always blocks allow powerful statements

- **if .. then .. else**
- **case**

**Difference
between
Synchronous
and
Asynchronous
Sequential
Circuits**

SYNCHRONOUS CIRCUIT	ASYNCHRONOUS CIRCUIT
All the State Variable changes are synchronized with a universal clock signal.	The State Variables are not synchronized to change simultaneously and may change at anytime irrespective of each other to achieve the next Steady Internal State
Since all the Internal State changes are in the strict control of a master clock source they are less prone to failure or to a race condition and hence are more reliable.	Since there is no such universal clock source, the internal state changes as soon as any of the inputs change and hence are more prone to a race condition.
Timings of the internal state changes are in our control.	The changes in the internal state of an asynchronous circuit are not in our control.


Verilog Language Features

Sequential Circuits

32-bit counter with synchronous reset:

```
module simple_counter(clk, rst, count);  
  input clk, rst;  
  output [31:0] count;  
  reg [31:0] count;  
  
  always @(posedge clk)  
  begin  
    if(rst)  
      count = 32'b0;  
    else  
      count = count + 1;  
  end  
endmodule
```

 Because we must have
a *reg* type var at LHS
Otherwise: compiler error



If *rst* is high, reset
occurs at the positive
edge of the next clock.

How to make
this async.?


Any variable assigned
within the *always* block
must be of type *reg*.

Verilog Language Features

Sequential Circuits

Solution: 32-bit counter with asynchronous reset:
 
```
module simple_counter(clk, rst, count);  
    input clk, rst;  
    output [31:0] count;  
    reg [31:0] count;  
  
    always @(posedge clk or posedge rst)  
    begin  
        if(rst)  
            count = 32'b0;  
        else  
            count = count + 1;  
        end  
    endmodule
```



Reset occurs whenever
rst goes high.

Non-blocking and Blocking Statements

Non-blocking

```
always @ (a)
begin
    a <= 2'b01;
    b <= a;
    // all assignments are made here
    // b is not (yet) 2'b01
end
```

- Values are assigned at the end of the block.
- All assignments are made in parallel, process flow is **not-blocked**.

Blocking

```
always @ (a)
begin
    a = 2'b01;
    // a is 2'b01
    b = a;
    // b is now 2'b01 as well
end
```

- Value is assigned immediately.
- Process waits until the first assignment is complete, it **blocks** progress.

Blocking statements allow sequential descriptions


How to Simulate Verilog Module(s)

Testbench: provides stimulus to Unit-Under-Test (UUT) to verify its functionality, captures and analyzes the outputs.


Requirements:

Inputs and outputs need to be connected to the test bench

Our Verilog module

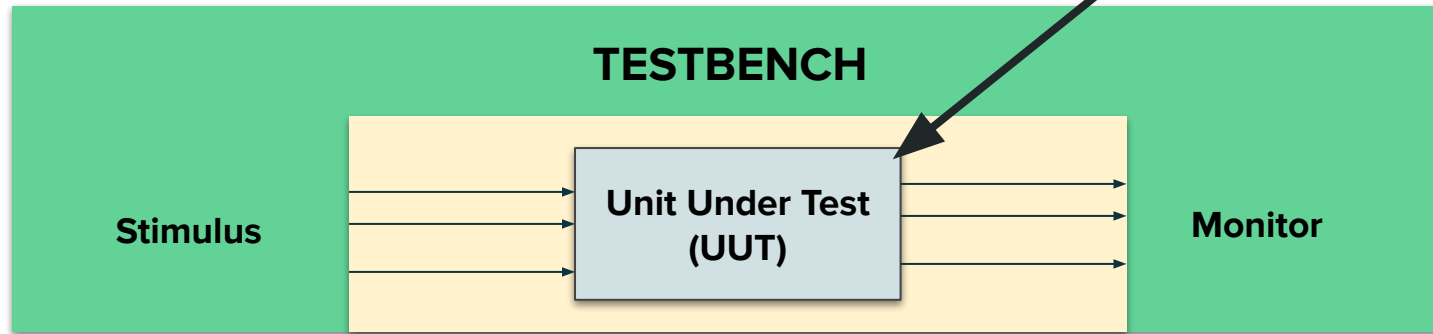

 How to Simulate Verilog Module(s) **Example**




Suppose we want to design
and simulate this circuit.

We can choose
either *behavioral*
or *structural*
design.

How to Simulate Verilog Module(s) **Example**

 Let's choose structural gate-level design:




```
module function_Y (A, B, C, D, E, F, Y);  
    input A, B, C, D, E, F;  
    output Y;  
    wire t1, t2, t3, Y;  
    //structural description
```

Which gates do we need, and what will the connections be?

```
endmodule
```

How to Simulate Verilog Module(s) **Example**

 Let's choose structural gate-level design:




```
module function_Y (A, B, C, D, E, F, Y);  
    input A, B, C, D, E, F;  
    output Y;  
    wire t1, t2, t3, Y;  
    //structural description  
    nand G1(t1, A, B);
```

```
endmodule
```

How to Simulate Verilog Module(s) **Example**

 
Let's choose structural gate-level design:



```
module function_Y (A, B, C, D, E, F, Y);  
    input A, B, C, D, E, F;  
    output Y;  
    wire t1, t2, t3, Y;  
    //structural description  
    nand G1(t1, A, B);  
    and G2(t2, C, ~B, D);  
    nor G3(t3, E, F);  
    nand G4(Y, t1, t2, t3);  
endmodule
```

How to Simulate Verilog Module(s) **Example**

 
Let's choose structural gate-level design:



```
module function_Y (A, B, C, D, E, F, Y);  
    input A, B, C, D, E, F;  
    output Y;  
    wire t1, t2, t3, Y;  
    //structural description  
    nand G1(t1, A, B);  
    and G2(t2, C, ~B, D);  
    nor G3(t3, E, F);  
  
endmodule
```

How to Simulate Verilog Module(s) **Example**

 Let's choose structural gate-level design:




Now we need to provide stimulus and monitor the outputs - **TESTBENCH**

```
module function_Y (A, B, C, D, E, F, Y);  
    input A, B, C, D, E, F;  
    output Y;  
    wire t1, t2, t3, Y;  
    //structural description  
    nand G1(t1, A, B);  
    and G2(t2, C, ~B, D);  
    nor G3(t3, E, F);  
    nand G4(Y, t1, t2, t3);  
endmodule
```


Saved as
function_Y_testbench.v

How to Simulate Verilog Module(s) **Example**

TESTBENCH

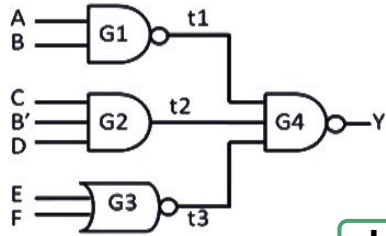

Saved as
function_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
module function_Y_testbench;
```


```
endmodule
```

Note there are no
ports in a testbench!

Saved as
function_Y_testbench.v

How to Simulate Verilog Module(s) **Example**

TESTBENCH

 

Saved as
function_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
module function_Y_testbench;
    reg A, B, C, D, E, F;
    wire Y;
```


Vars **MUST** be
declared as **reg**
Output as **wire**

```
endmodule
```

Saved as
function_Y_testbench.v

How to Simulate Verilog Module(s) **Example**

TESTBENCH

 

Saved as
function_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
module function_Y_testbench;
    reg A, B, C, D, E, F;
    wire Y;
```


```
function_Y UUT(A, B, C, D, E, F, Y);
```

```
endmodule
```

Initialize Unit
Under Test (UUT)

How to Simulate Verilog Module(s) Example

TESTBENCH

 

Saved as
function_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
`include "function_Y.v"
module function_Y_testbench;
    reg A, B, C, D, E, F;
    wire Y;

    function_Y UUT(A, B, C, D, E, F, Y);


    initial
        begin
            //initial block - gets executed once

        end
endmodule
```

Saved as
function_Y_testbench.v

How to Simulate Verilog Module(s) Example

TESTBENCH

 

Saved as
function_Y.v

Unit Under Test

```
module function_Y (A, B, C, D, E, F, Y);
    input A, B, C, D, E, F;
    output Y;
    wire t1, t2, t3, Y;
    //structural description
    nand G1(t1, A, B);
    and G2(t2, C, ~B, D);
    nor G3(t3, E, F);
    nand G4(Y, t1, t2, t3);
endmodule
```

```
`include "function_Y.v"
module function_Y_testbench;
    reg A, B, C, D, E, F;
    wire Y;

    function_Y UUT(A, B, C, D, E, F, Y);

    initial
        begin
            #10 A = 0; B = 0; C = 0; D = 0; E = 0; F = 0;
            #10 A = 1; B = 0; C = 1; D = 1; E = 0; F = 0;
            #10 A = 0; B = 1;
            #10 F = 1;
            #10 $finish;
        end
endmodule
```

Stimulus

How to Simulate Verilog Module(s) **Example**


Results can be viewed as waveforms:



How to Simulate Verilog Module(s) **Example**

We can also monitor the changes and print them to the console using *\$monitor*:
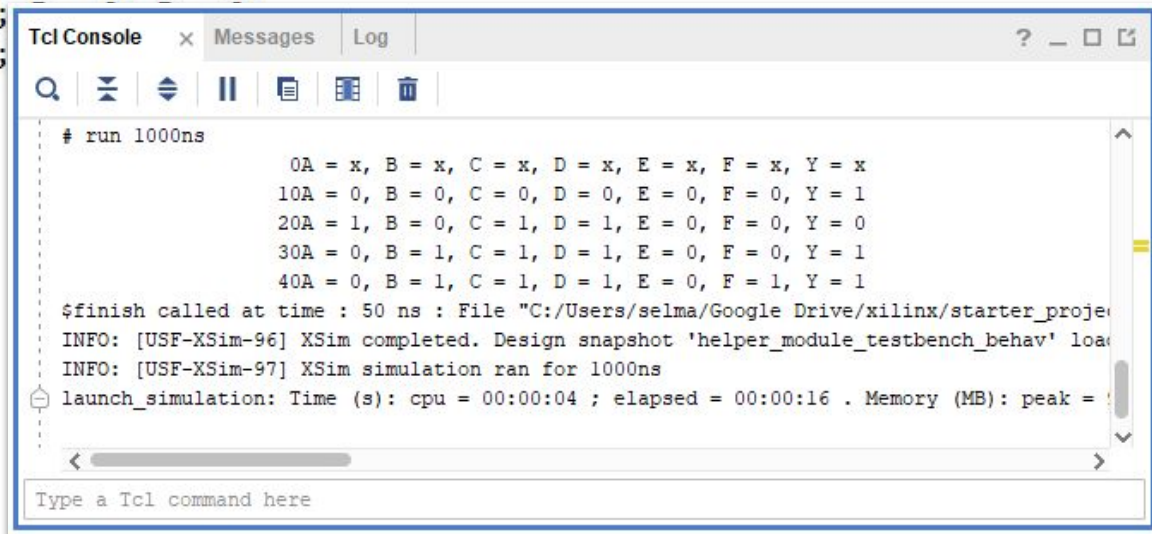
```
initial
begin
    $monitor ($time, "A = %b, B = %b, C = %b, D = %b, E = %b, F = %b, Y = %b", A, B, C, D, E, F, Y);
    #10 A = 0; B = 0; C = 0; D = 0;
    #10 A = 1; B = 0; C = 1; D = 1;
    #10 A = 0; B = 1;
    #10 F = 1;
    #10 $finish;
end
```



We can also use *\$dumpfile* to dump variable changes to a file.